

Component-by-Component Wiring List:

A. Rain Sensor (FC-37 or similar)

These sensors usually consist of a sensing board and a small driver board. The driver board typically has four pins:

1. **VCC (Sensor Board):** Connect to Arduino 5V.
2. **GND (Sensor Board):** Connect to Arduino GND.
3. **AO (Analog Out):** Connect to Arduino Pin A0.
4. *(DO (Digital Out): Not used in this code).*

B. Piezo Buzzer

- **Positive (+) Terminal (Long Leg):** Connect to Arduino Pin 11.
- **Negative (-) Terminal (Short Leg):** Connect to Arduino GND.

(You should also place a 220Ω resistor in series with the buzzer for protection).

C. L298N Motor Driver

The L298N module has three terminals on one side (Power) and two terminals on another (Motor Outputs). The control pins are on a separate header.

Power Terminals:

1. **12V (or VCC):** Connect to the **POSITIVE (+) terminal of your external battery** (e.g., a 9V battery). *This powers the motor.*
2. **GND:** Connect to the **NEGATIVE (-) terminal of your external battery AND Arduino GND.**
3. **+5V Out:** *Not used. (This can output 5V to power an Arduino if you aren't using USB, but for now, leave it disconnected).*

Control Pins (Input):

- **IN1 (Input 1):** Connect to Arduino Pin 8.
- **IN2 (Input 2):** Connect to Arduino Pin 9.
- **ENA (Enable A) / ENB (Enable B):** Make sure the jumpers are installed on these. This keeps the outputs "enabled" for simple bidirectional control.

Motor Output Terminals:

- **OUT1:** Connect to one lead of the DC motor.
- **OUT2:** Connect to the other lead of the DC motor.